



Join 'VIT Question Papers Today' By Scanning The QR Or By Simply Searching It On Telegram App.



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Continuous Assessment Test – I

Winter Semester 2019-20

SCAN ME

Programme Name & Branch: B.Tech – EEE & EIE






Date & Slot: 19-1-2020 & A1

Course Name & Code: Semiconductor Devices & Circuits –EEE2002

Exam Duration: 1.5 Hrs

Maximum Marks: 50


Faculty Name : Prof. G.K.Rajini/Prof.G. Vidhya Sagar /Prof.M.N. Venkataraman/Prof. Washima Tasnin

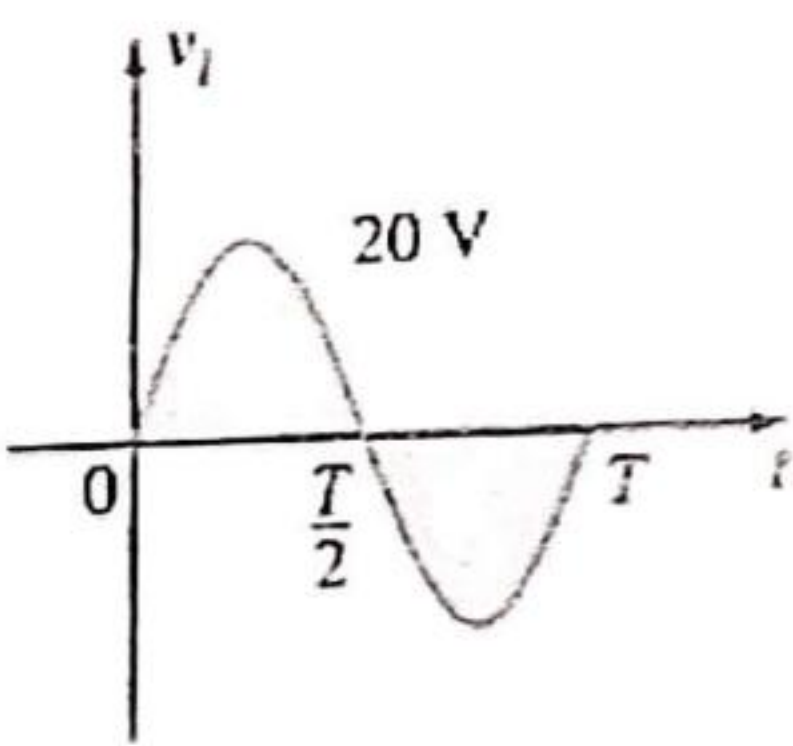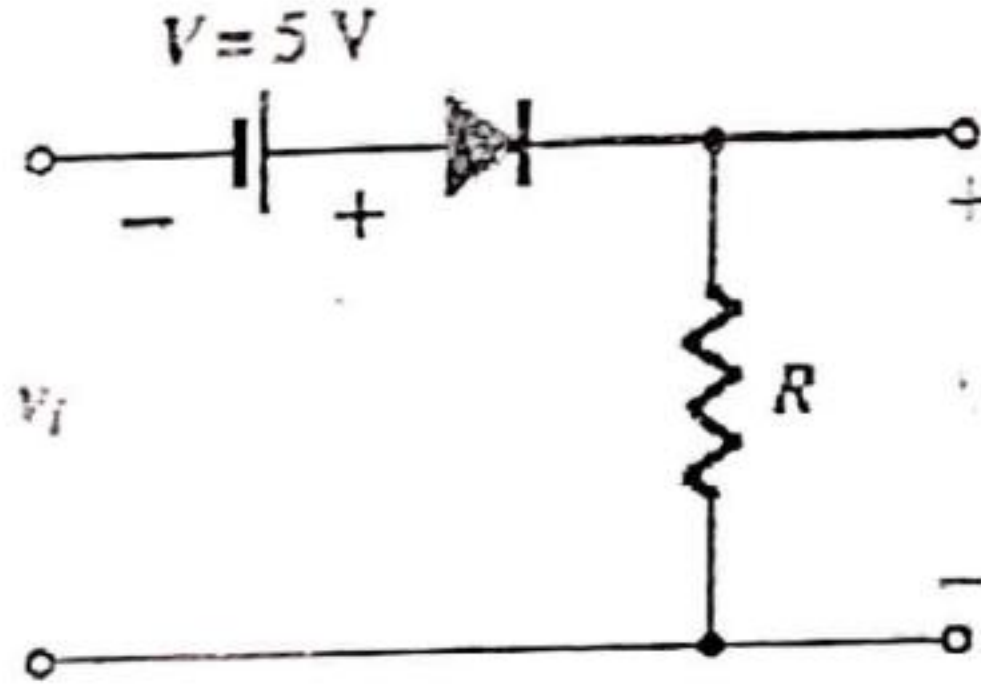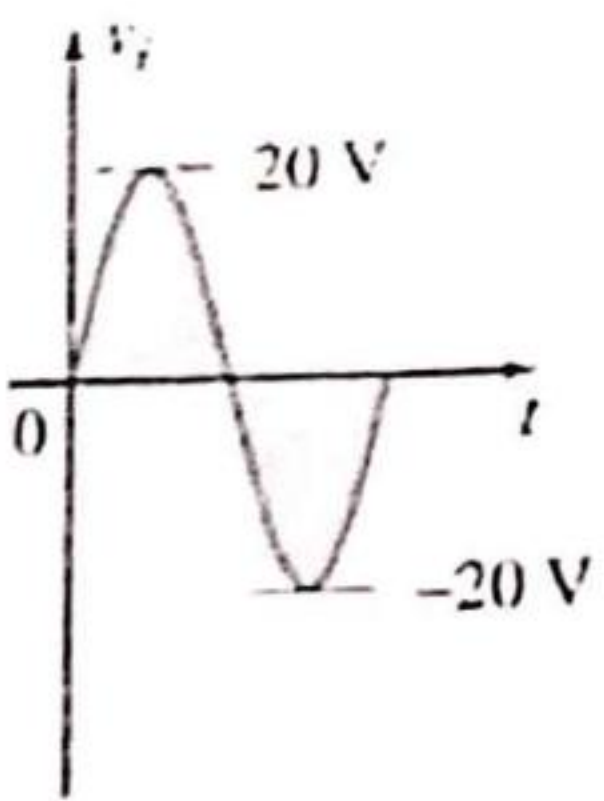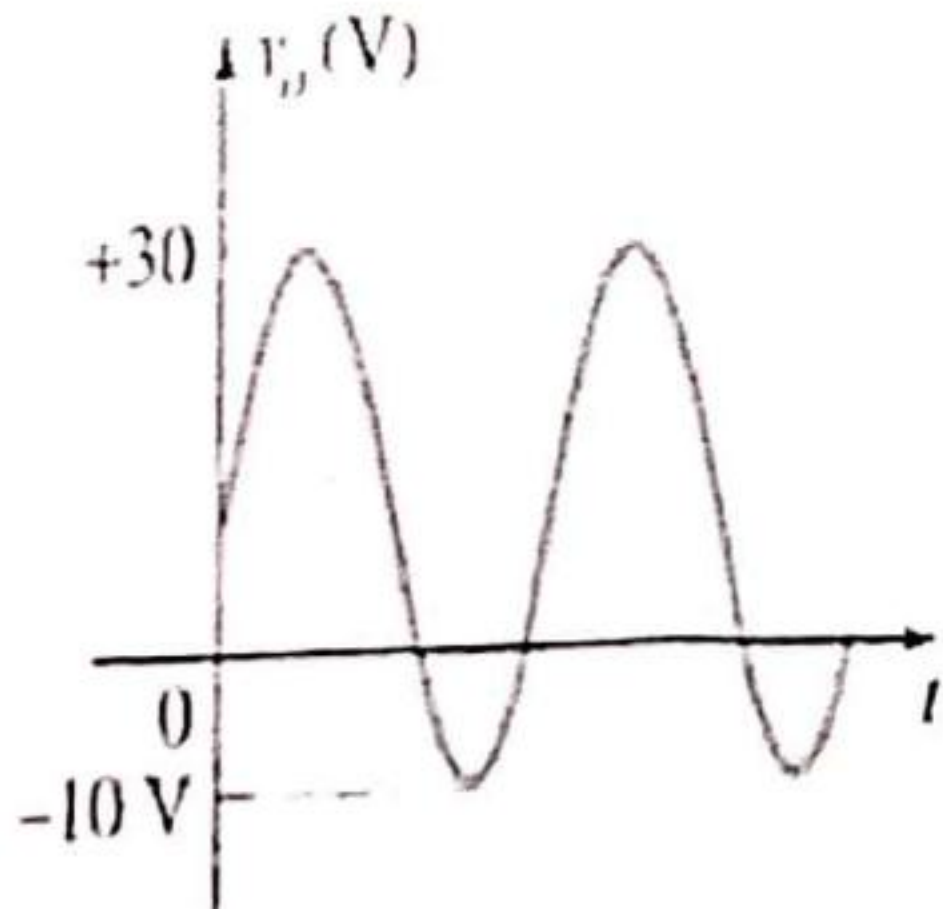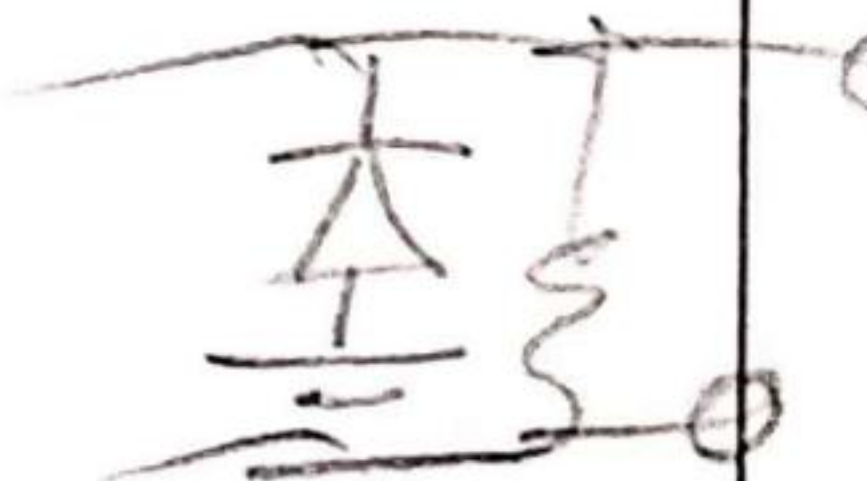S.No.	Questions
1.	<p>With necessary explanation discuss the characteristics of PN junction diode and elaborate on Drift and Diffusion currents in it.</p> <p style="text-align: right;">[10Marks]</p>
2. a.	<p>For the given input signal & Clipper circuit, sketch the output voltage v_o for the following specifications shown below.</p> <p style="text-align: right;">[5Marks]</p> <div style="display: flex; justify-content: space-around; align-items: center;">   </div>
2.b.	<p>Design a clamper circuit using PN diode for the given input and output sinusoidal signal shown below.</p> <p style="text-align: right;">[5 Marks]</p> <div style="display: flex; justify-content: space-around; align-items: center;">    </div> <p style="text-align: center; margin-top: 20px;">20</p>

3.

The Silicon PN diode in the circuit given below is specified with following voltages. Find the currents flowing through the diodes D_1 and D_2 .

[10Marks]

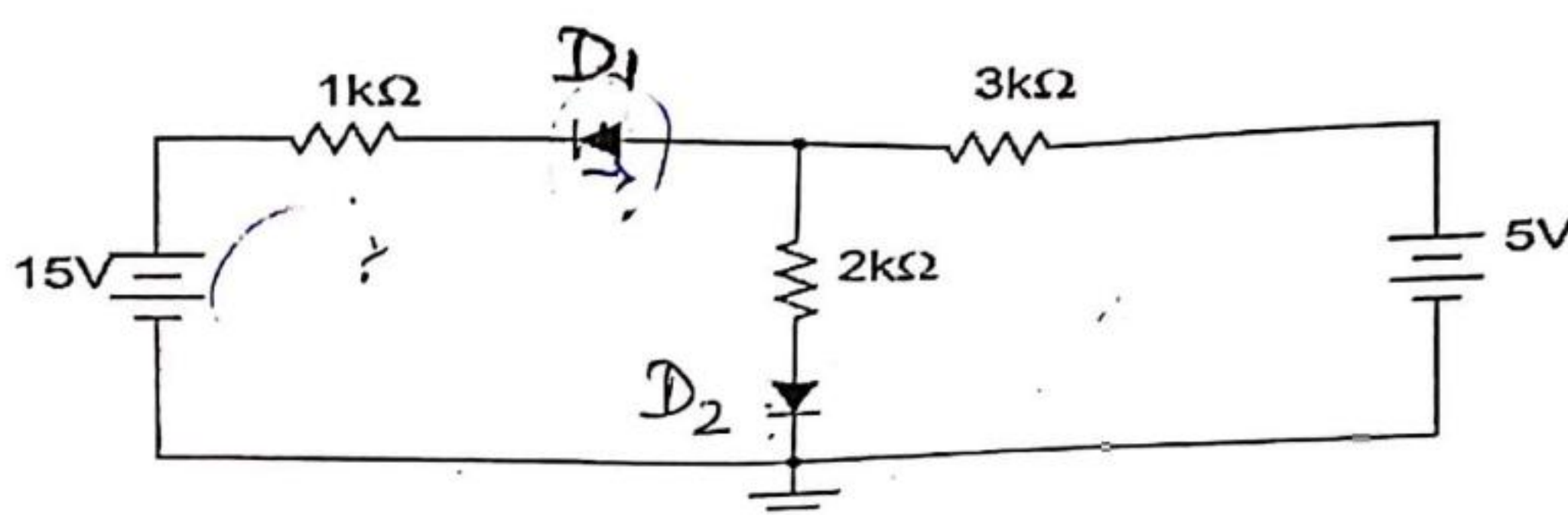

4.

Explain the operation of BJT and explain its input & output characteristics of CE configuration and various operating regions.


[10Marks]

5.

Determine the operating region of transistor and also the currents and voltages for the given circuit below. Given $\beta = 100$ and $V_{BE(on)} = 0.7V$

i) I_B ii) I_C iii) I_E iv) V_{CE} v) V_{CB}

[10 Marks]

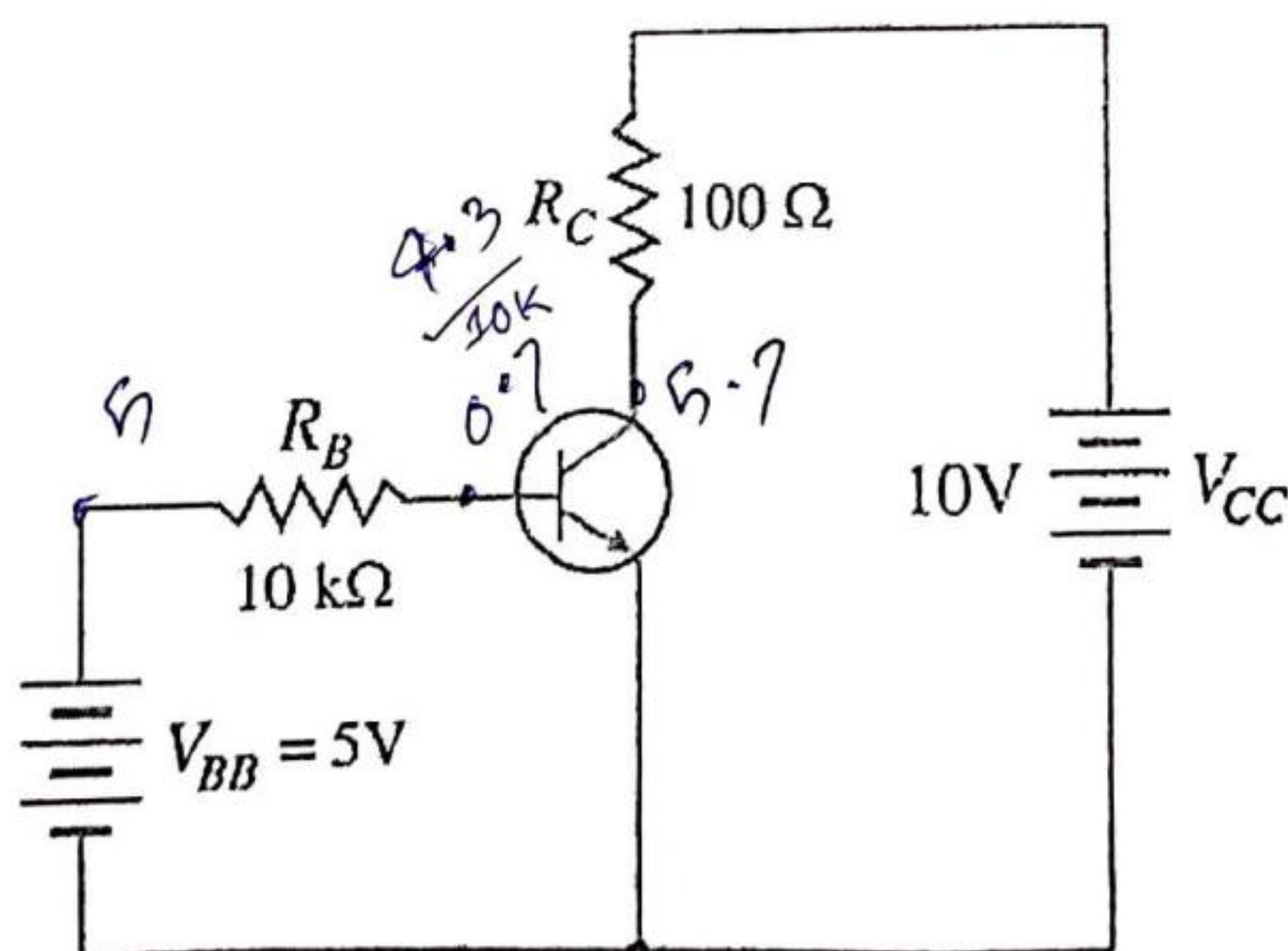

0.43 mA



Join 'VIT Question Papers Today' By Scanning The QR Or By Simply Searching It On Telegram App.

SCAN ME



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

SCHOOL OF ELECTRICAL ENGINEERING
CAT I

Discipline : B.Tech
Subject Code : EEE2001
Subject Name : Network Theory
Slot : B1+TB1

Semester : Winter 2020
Max. Marks : 50
Time : 1 ½ hours
Date: :20.01.2010

Instructions: Answer ALL questions

- 1 Use the node-voltage method to find the branch currents I_a , I_b , I_c and I_x in the circuit shown in Fig. 1. [10]

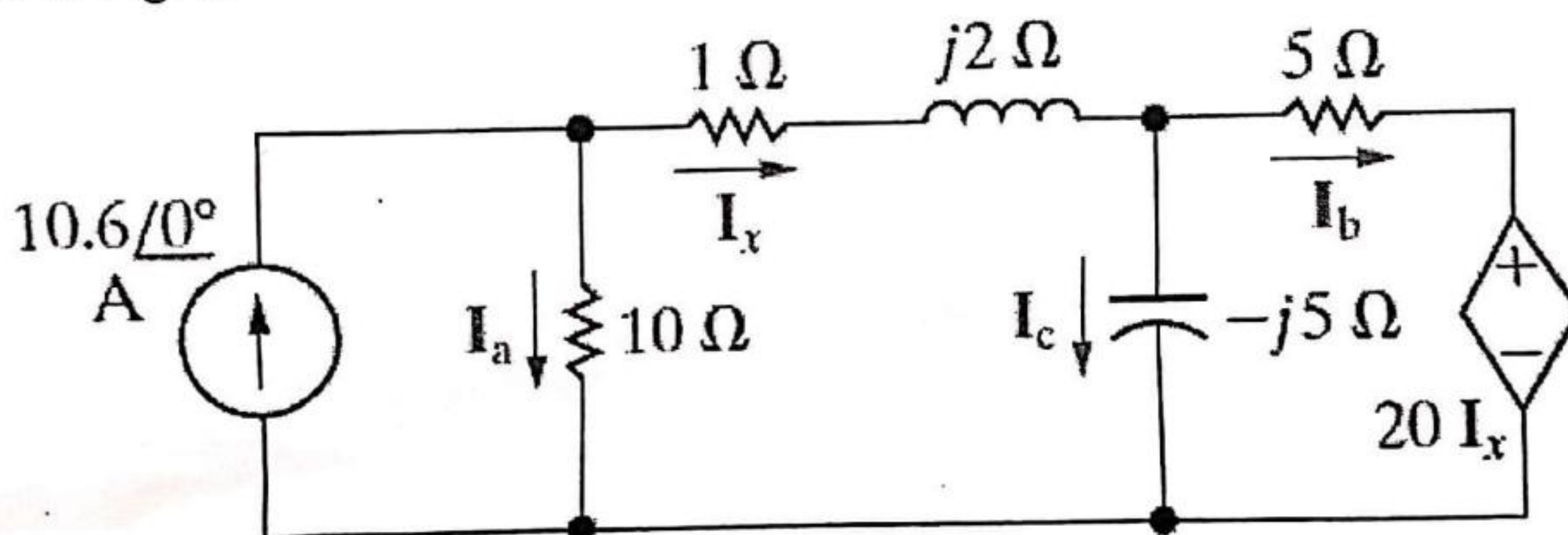


Fig. 1

- 2 In Fig. 2, the resistor R_L is adjusted until it absorbs the maximum average power. Calculate R_L and the maximum average power absorbed by it. [10]

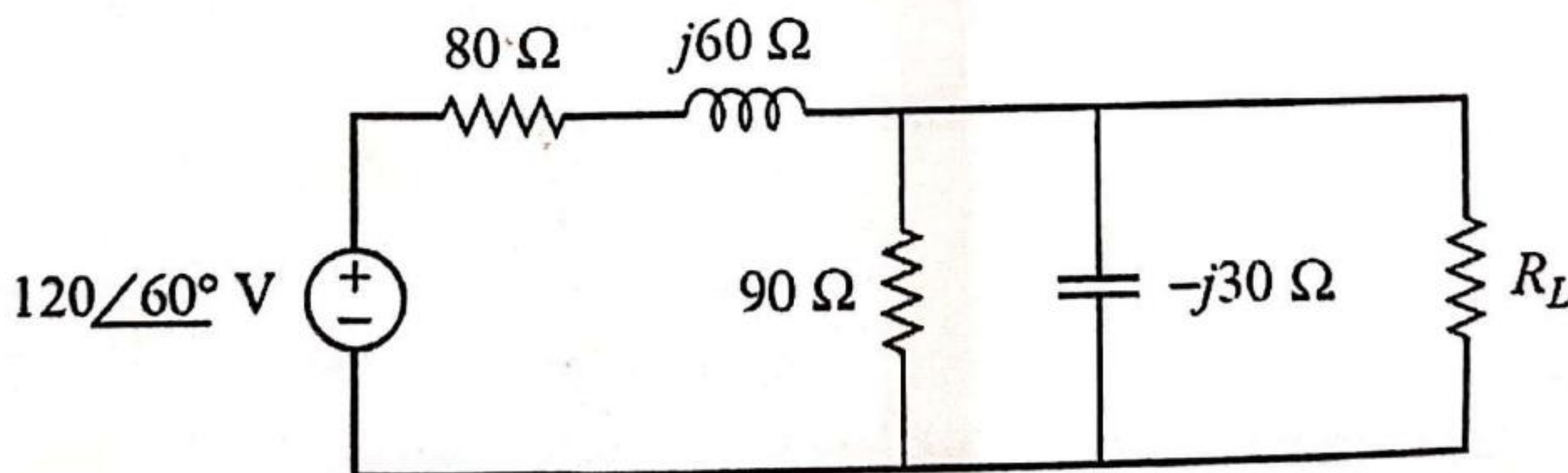


Fig. 2.

- 3 Solve for $v_o(t)$ in the circuit of Fig. 3 using the superposition principle. [10]

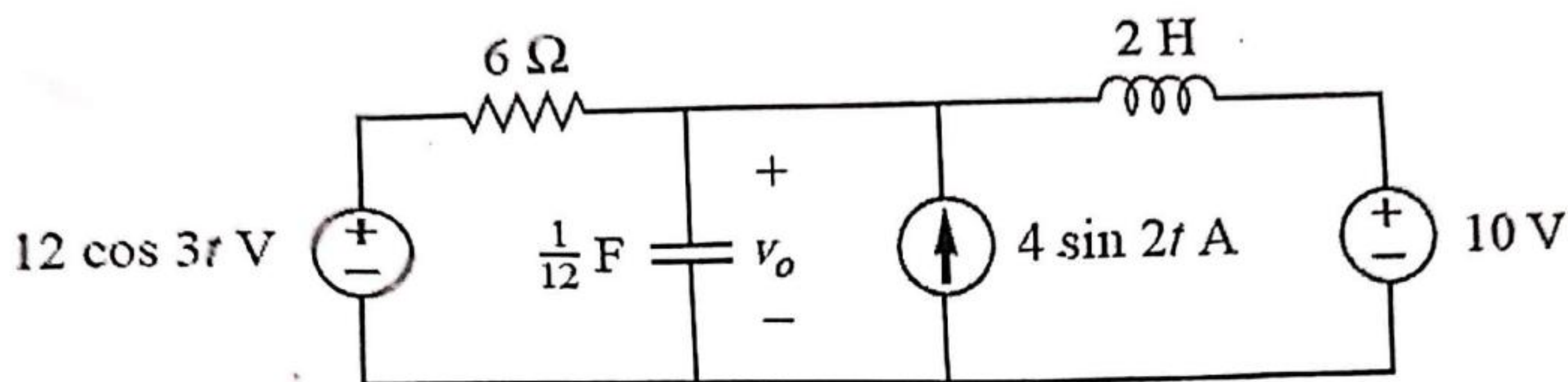


Fig. 3

- 4 Determine $i_o(t)$ in the circuit in Fig. 4. assuming zero initial conditions. [10]

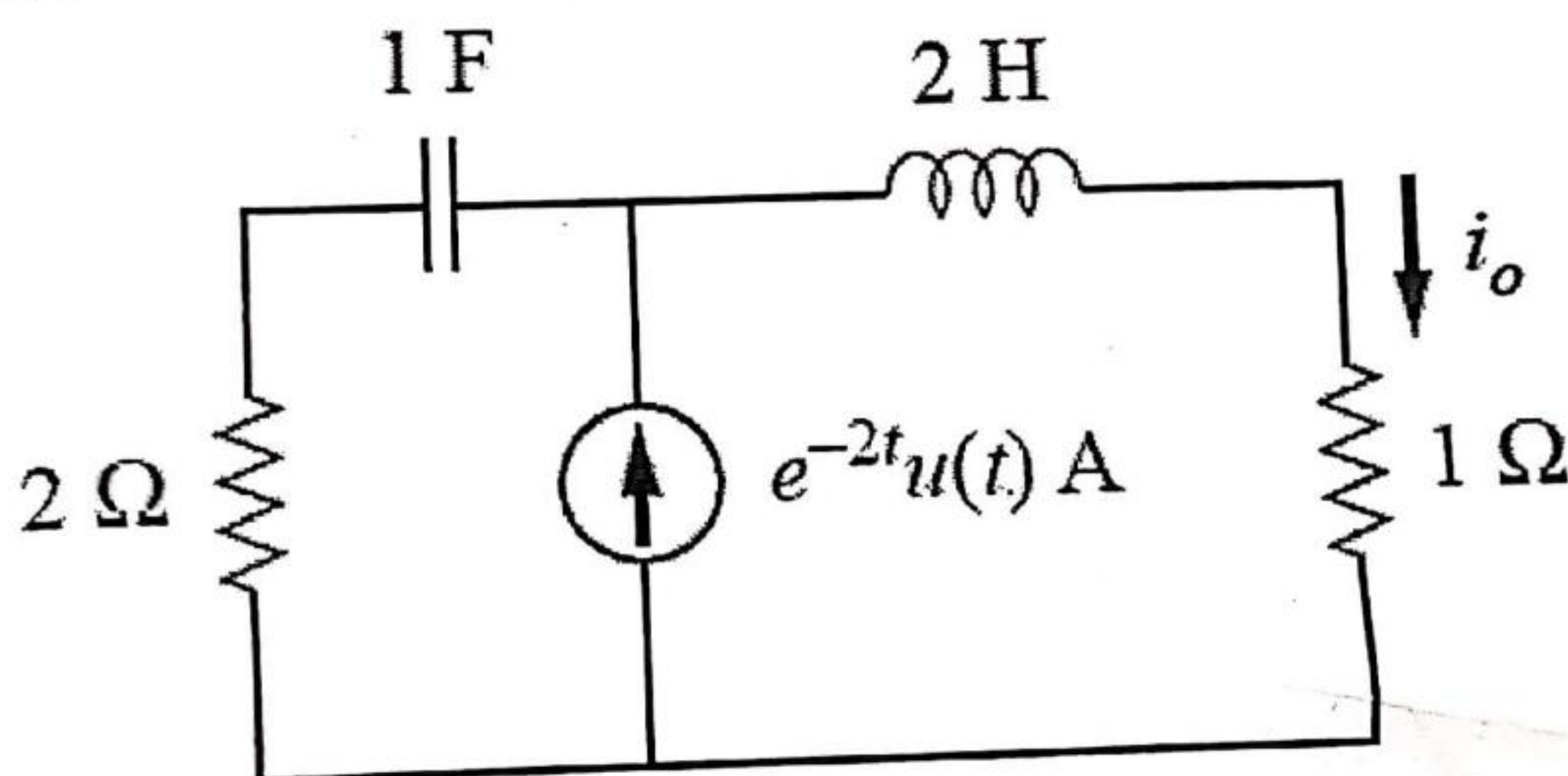


Fig. 4

- 5 Consider the parallel RLC circuit of Fig. 5. Find $v(t)$ and $i(t)$ given that $v(0) = 5$ V and $i(0) = -2$ A. [10]

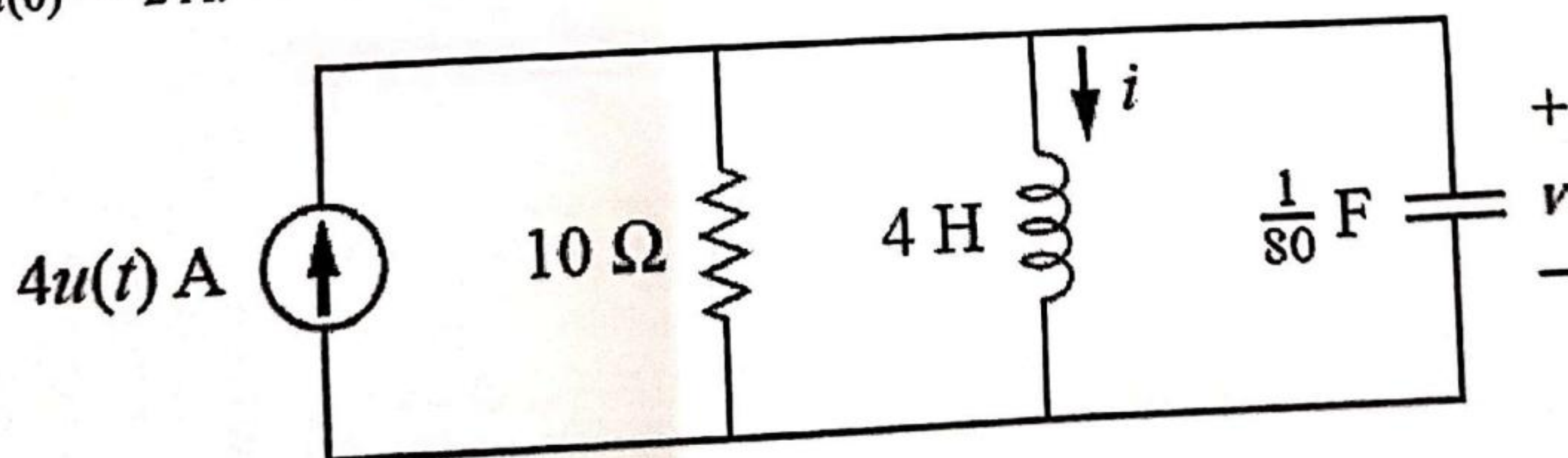


Fig. 5

-2

8



SCAN ME

Join ' VIT Question Papers Today ' By Scanning The QR Or By Simply Searching It On Telegram App.



VIT

Vellore Institute of Technology
Chennai 605 019, India

Continuous Assessment Test – I

Programme Name & Branch : B.TECH (EEE,ECE,EIE and MECH)

Course Name & Code : Engineering Electromagnetics, EEE 1004

Slot: CI+TCI

Exam Duration: 1:30 Min

Max. Marks: 50

Faculty: Dr. V. Indragandhi , Dr. Venkatesh .S, Dr. C. Rani and Dr. Himadri Lala

Answer all questions (5*10 = 50 Marks).

No.	Question
1.	Express the Cartesian unit vector \hat{a}_x in Spherical coordinate systems at the point T (2,3,-4).
2.	State Gauss's Divergence Theorem. Verify Gauss's Divergence Theorem for the vector field $\vec{A} = xy^2\hat{a}_x + y^3\hat{a}_y + y^2z\hat{a}_z$ defined on the closed cubic region defined by $0 \leq x \leq 1$, $0 \leq y \leq 1$, $0 \leq z \leq 1$.
3	Point charges 5 nC and 2 nC each are located at A (2, 0, 4), B (-3, 0, 5) respectively. a) Determine the force on a 1 nC point charge which is located at C (1,3,-7) b) Find the electric field at C (1,3,-7)
4	A point charge 100 pC is located at (4, 1, -3) while the x-axis carries a line charge of 2 nC/m. If the plane $z = 3$ also carries charge of 5 nC/m ² , calculate E at (1,1,1).
5	Determine the electric field everywhere due to a uniformly charged sphere of radius 'x' and total charge q. Make a rough plot of the magnitude of the electric field with respect to the distance from the center of the sphere.